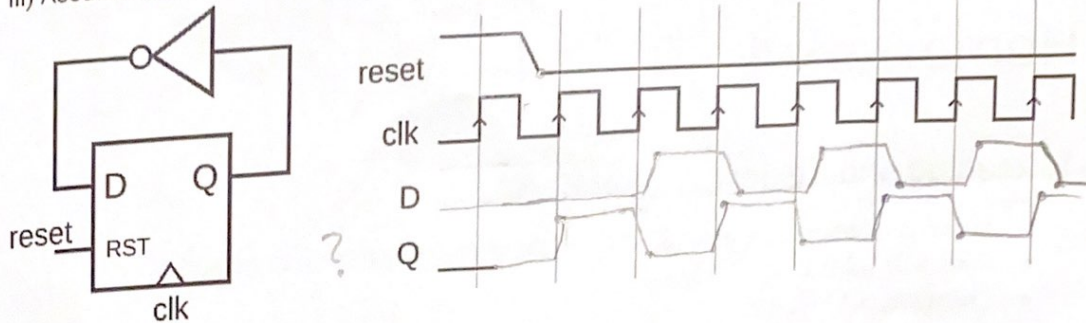


iii) Assume reset is active high **and** synchronous. Sketch the waveforms for D and Q below.




2. Verilog Skillbuilding

a) Verilog to Schematic


For each output, draw an equivalent gate level schematic ***and*** write a phrase or sentence describing what that output does in terms of the inputs.

```
module mystery(a,b,c, out);
  input wire a, b, c;
  output logic out[3:0];
  always_comb begin
    out[0] = b ? a : c;
    out[1] = (~a & b) | (~b & a);
    out[2] = c | ( b & c);
  end
  logic d;
  always_comb d = b ? a : 1'b0;
  always_ff @(posedge c) begin
    out[3] <= d;
  end
endmodule
```


out[0]:

 


out[1]:

 

out[2]:



out[3]:

 

b) Schematic to Verilog

Create this module as part of your zipped submission. There's a testbench to go with it so you can see what it does (it's not an obviously useful circuit but it has some interesting use cases).

